

Project

You are required to design an 8-bit adder. You should choose one of the following adder architectures:

- Brent-kung adder
- Sklansky adder
- Koggestone adder
- Han-carlson
- Knowles
- Ladner-Fischer

You are required to perform the following:

- 1- Automatic approach
 - Write Verilog HDL description of the adder
 - Write a testbench and verify the correctness of your design.
 - Synthesize your design using genus
 - Place and route your design using innovus.
 - Post-layout Verilog simulation.
 - Determine the maximum delay of the adder.
- 2- Manual approach
 - Write Verilog HDL code for the gray cell, black cell, xor cell, pg cells
 - Design scaling of all cells
 - Design layout of all cells for all required scalings
 - Write structural Verilog HDL code for the adder.
 - Perform place and route for the adder using innovus
 - Perform post-layout simulation
 - Determine the maximum delay of the adder
- 3- Compare automatic approach and manual approach in terms of speed and area.

You should use 180 nm technology using TSMC technology library.

List of deliverables:

- Complete Verilog code
- Complete layout
- Report that contains:
 - o Overview of the adder
 - o Design details (how you selected scaling)
 - o Simulation results

Deadline:

20 – May - 2022